

Computer organization

Chapter 5

學號：

姓名：

1. (18%) Describe the effect that a single stuck-at-0 fault (i.e., regardless of what it should be, the signal is always 0) would have for the signals shown below, in the multiple-cycle datapath in Figure 2. Which instructions, if any, will not work correctly? Explain why.
 - A. RegWrite = 0
 - B. MemRead = 0
 - C. MemWrite = 0
 - D. IRWrite = 0
 - E. PCWrite = 0
 - F. PCWriteCond = 0

<sol>

- a. **RegWrite** = 0: All R-format instructions, in addition to `sw`, will not work because these instructions will not be able to write their results to the register file.
- b. **MemRead** = 0: None of the instructions will run correctly because instructions will not be fetched from memory.
- c. **MemWrite** = 0: `sw` will not work correctly because it will not be able to write to the data memory.
- d. **IRWrite** = 0: None of the instructions will run correctly because instructions fetched from memory are not properly stored in the IR register.
- e. **PCWrite** = 0: Jump instructions will not work correctly because their target address will not be stored in the PC.
- f. **PCWriteCond** = 0: Taken branches will not execute correctly because their target address will not be written into the PC.

2. (10%) Please add any necessary datapaths and control signals to include the instruction **beq (branch on equal)** to the single-cycle datapath shown in Figure 1.
3. (18%) According to the single-cycle datapath in Figure 1, please fill in the blanks in the following table of control signals

Instruction	RegDst	ALUSrc	MemtoReg	RegWrite	MemRead	MemWrite	Branch	ALUOp1	ALUOp0
R-format	1	0	0	1	0	0	0	1	0
lw	0	1	1	1	1	0	0	0	0

4. (18%) Consider the following machines, and compare their performance using the data below.

Instruction	Frequency
Loads	30%
Stores	20%
R-type	40%
Branch/Jump	10%

M1: The multicycle datapath of Chapter 5 with a **3.8 GHz** clock.

M2: A machine like the multicycle datapath of Chapter 5, except that register updates are done in the same clock cycle as a memory read or ALU operation. Thus in Figure 3, states 6 and 7 and states 3 and 4 are combined. This machine has a **3.5 GHz** clock, since the register update increase the length of the critical path.

M3: A machine like M2 except that effective address calculations are done in the same clock cycle as a memory access. Thus states 2, 3, and 4 can be combined, as can 2 and 5, as well as 6 and 7. This machine has a **2.8 GHz** clock because of the long cycle created by combining address calculation and memory access.

1. Please calculate the average CPI of each machine.

Find out which of the machine is fastest.

<sol>

1.

M1	
Instruction	cycle
Loads	5
Stores	4
R-type	4
Branch/Jump	3

M2	
Instruction	cycle
Loads	4
Stores	4
R-type	3
Branch/Jump	3

M3	
Instruction	cycle
Loads	3
Stores	3
R-type	3
Branch/Jump	3

M1: Average CPI = 4.2 the average time of excuting a instruction:

$4.2/3.8=1.105$

M2: Average CPI = 3.5 the average time of excuting a instruction: $3.5/3.5=1$

M3: Average CPI = 3 the average time of excuting a instruction: $3/2.8=1.071$

2. The M2 machine is fastest!!

5. (22%) Note that some control signals are absent in the finite state machine of Figure 3. Please finish Figure 3 according to the multicycle datapath of Figure 2. In other word, please fill in the contents of state2, state4, state 9 in Figure 3.
6. (20%) We wish to design a method to detect exceptions, including *undefined instructions* and *arithmetic overflow*, and to transfer control to the appropriate state in the exception states. **Add any necessary datapaths and control signals to the multicycle datapath of Figure 2, and any necessary states and control signals to the finite state machine of Figure 3.** Not that *the exception address = 8000 0180*.

Figure 1

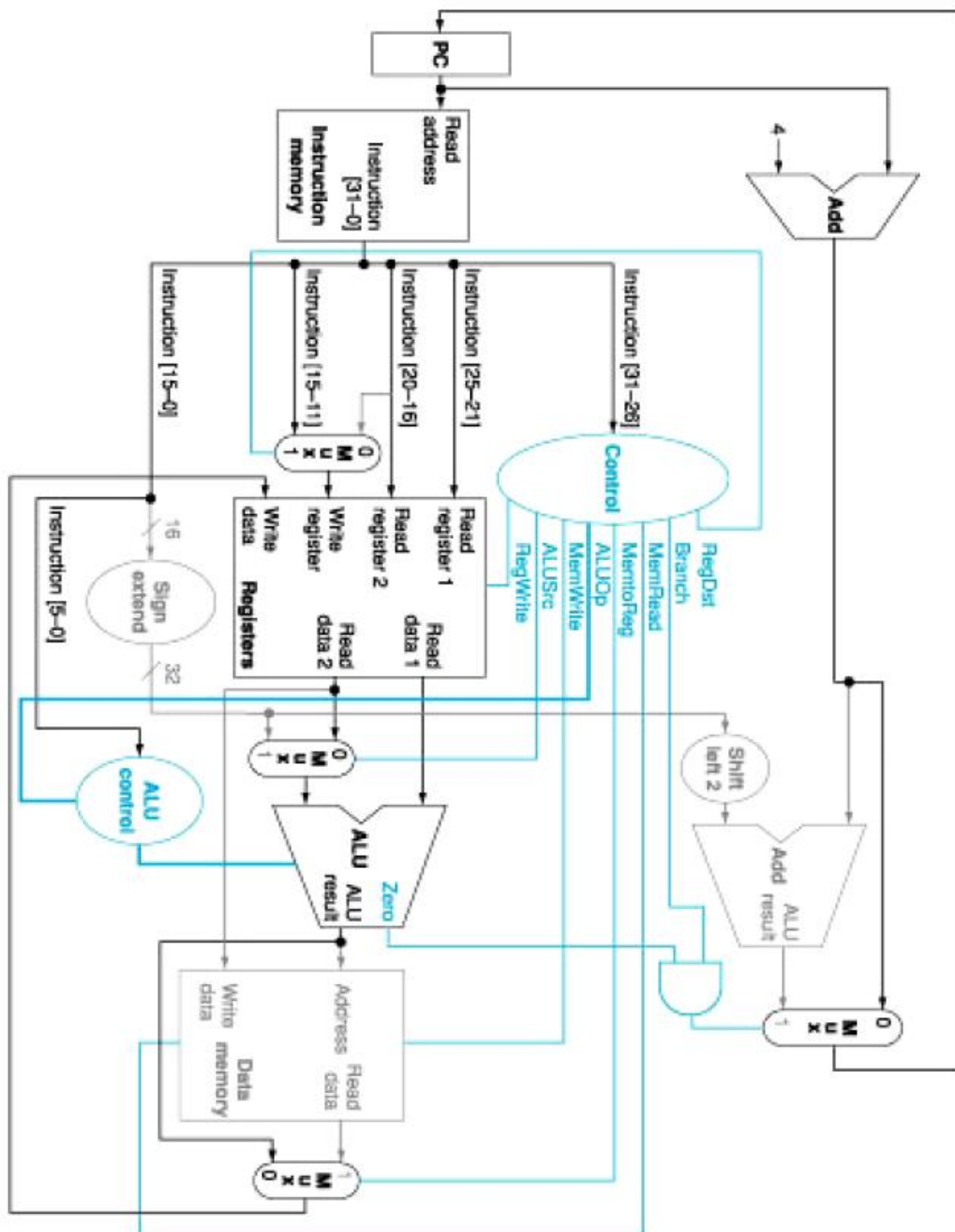


Figure 2

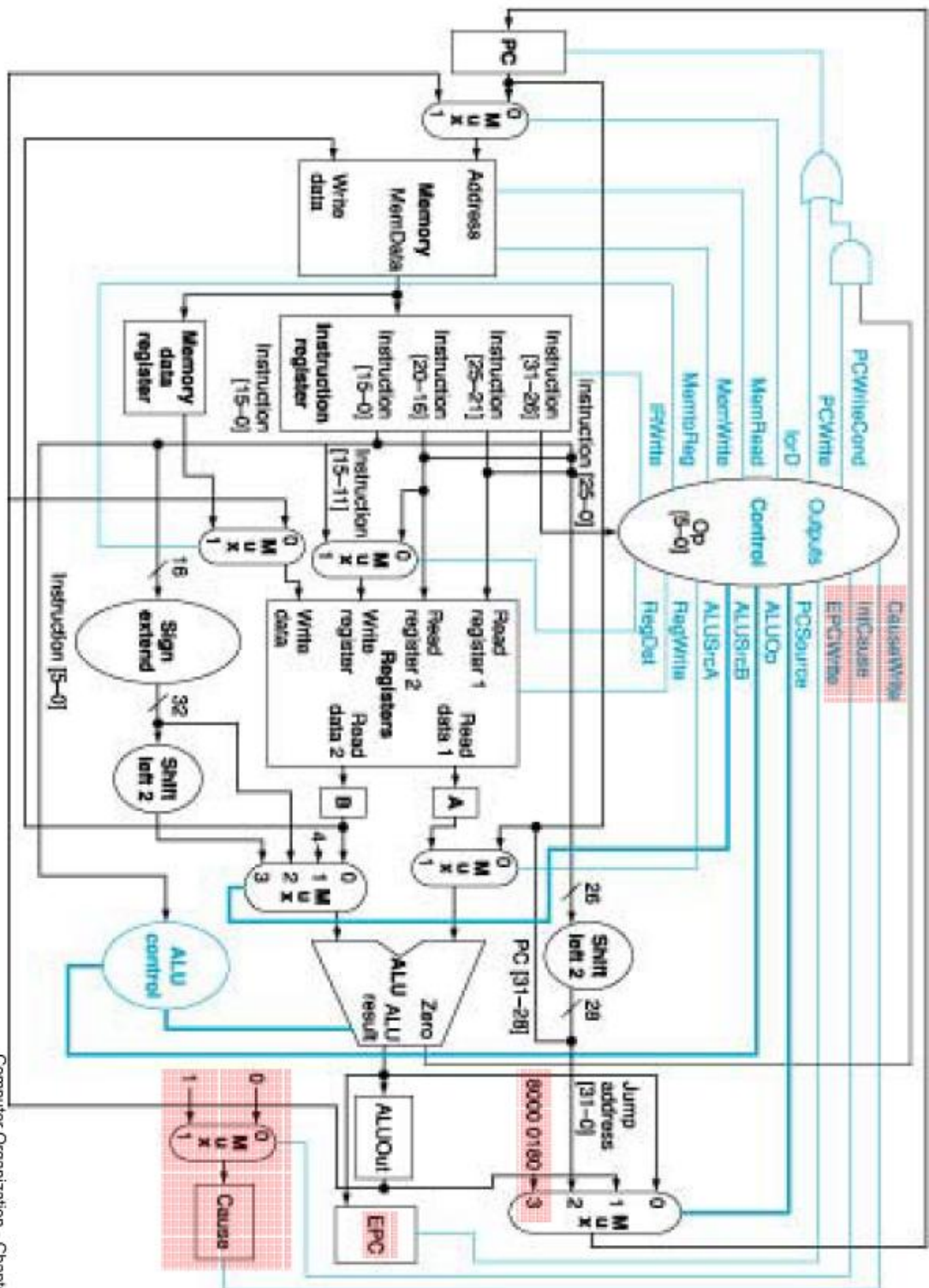


Figure 3

